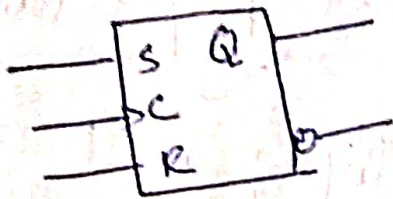


→ Flip-flops : → The storage elements in clocked sequence circuit are called flip-flops. A flip-flop is a binary cell capable of storing one bit of information. It has two outputs: one for normal value and one for the complement value of the ~~bit~~ bit stored in it. The difference between various flip-flops is in the no. of inputs they possess and in the manner in which the inputs affect the binary state.

## Types of flip-flops :-

### ① SR-flip-flop :- (Set-reset flip flop)

It has 3 inputs, labeled as S, R and C (clock). It has an output Q and its complemented output. The overhead shaped symbol in front of C is designated to be dynamic input.



Graphical symbol


S	R	T(Q+1)
0	0	Q: no change
0	1	0: clear to 0
1	0	1: set to 1
1	1	indeterminate

Characteristic table
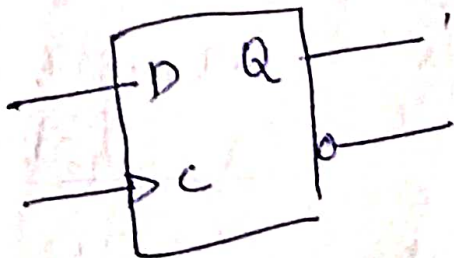
### ② D (Data) flip-flop :-

↳ slight modification of SR-flip flop

An SR flip-flop is converted to D-flip-flop by inserting an inverter b/w S and R assigning the symbol D to the ~~input~~ single input




D	T(Q+1)
0	0: clear to 0
1	1: set to 1
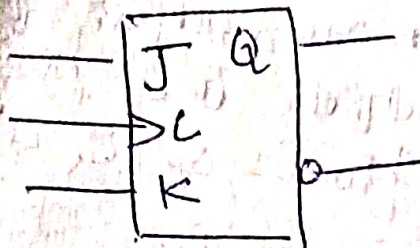
### ③ JK-flip-flop :-

→ refinement of SR flip-flop



Indeterminate condition of SR-type is defined by JK flip flop.




Graphical symbol

J	K	$t(Q+1)$
0	0	$t(Q)$ no change
0	1	0 clear to 0
1	0	1 Set to 1
1	1	$t'(Q)$ Complement
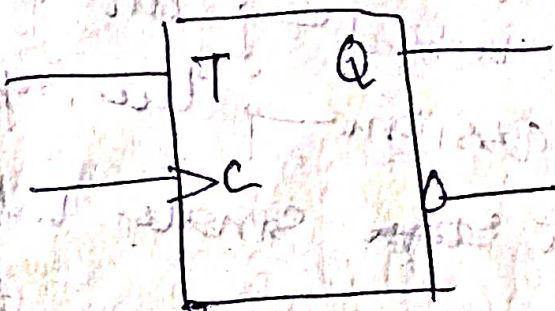
#### ④ T (toggle) flip-flop :-

→ Obtained from JK flip-flop when J and K are combined to provide a single input designated as T.



Graphical symbol

T	$T(Q+1)$
0	$Q(t)$ no change
1	$Q'(t)$ Complement

Characteristics table